

|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|

**B. Tech.**  
**(SEM III) ODD SEMESTER**  
**MAJOR EXAMINATION 2015 - 2016**

**DIGITAL CIRCUITS & LOGIC DESIGN**

Time: 3 Hrs.

Max. Marks: 40

Note: Answer all questions.

**Q.1 Attempt any three of the following from Unit-I. Q.1 (a) is compulsory.**

- a Find the value of x in the following: (3)
- (i)  $(653)_7 \times (523)_7 = (x)_7$  (ii)  $(D6C.5B)_{16} = (x)_4$
- (iii)  $x = (11010)_2 - (1101)_2$  subtract using 2's complement. (iv)  $(21340)_5 = (x)_{10}$
- b (3)
- (i) Prove that  $(A+B'+AB)(A+B')(A'B) = 0$ .
- (ii) Implement the Boolean function  $F = A'B'C + A'BC' + A'C'$  with NAND gate only.
- c Explain the block parity concept to check and correct the error in a single bit with example. (3)
- d Hamming code 101101101 is received at receiver end with even parity. Correct it if any errors. (4)

**Q.2 Attempt any three of the following from Unit-II. Q.2 (a) is compulsory.**

- a Design a 4 bit carry look ahead generator. (4)
- b Minimize the given Boolean function using K- map and implement the simplified function using NAND gates only.  $F(A,B,C,D) = \sum m(0,1,2,3,7,8,10) + d(5,6,11,15)$  (3)
- c Construct a 32x1 multiplexer with 4x1 multiplexers. Use block diagrams. (3)
- d Design a BCD to decimal decoder using the unused combinations of the BCD code as don't care conditions. (3)

**Q.3 Attempt any three of the following from Unit-III. Q.3 (a) is compulsory.**

- a Draw the schematic diagram of J-K flip – flop and describe its working. Write down its truth table (4)
- b Draw the logic diagram of a 2 to 4 line decoder with only NAND gates. Include an enable input. (3)
- c Design a synchronous counter which steers through the following states S4-S3-S6-S2-S5-S0 using J-K Flip Flops. (3)
- d Explain the working of 4-bit ripple counter with circuit diagram and timing diagram. (3)

**Q.4 Attempt any three of the following from Unit-IV. Q.4 (a) is compulsory.**

- a Draw and explain the working of universal shift register. (4)
- b A certain memory has a capacity of 8K\*32. How many bits are there in each word? How many words are being stored? How many address bits are required to uniquely identify each location? (3)
- c Differentiate between static and dynamic RAM on the basis of four parameters. (3)
- d What do you understand by fundamental mode of operation? Discuss different types of Hazards in Asynchronous sequential circuit by giving suitable example. (3)